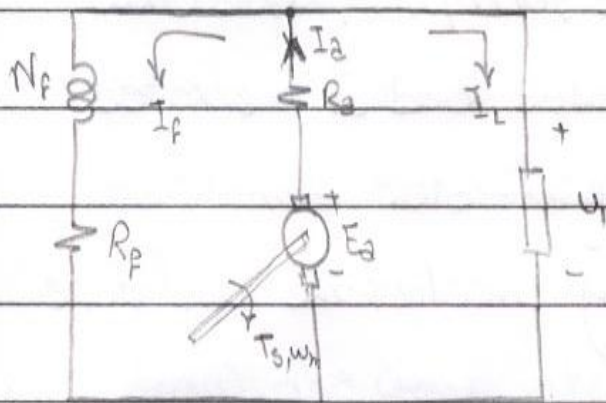


Direct Current Generator.

1. Shunt Generator.



$$P_{out} = V_t I_L \quad (\text{watt})$$

$$P_{in} = T_{sh} \omega_m \quad (\text{watt})$$


$$\omega_m = \frac{2\pi}{60} N_m \quad (\text{rad/sec})$$

equivalent ct. of shunt Gen.

$$I_a = I_f + I_L \quad (\text{Amp})$$

$$I_f = \frac{V_t}{R_f}$$

$$I_L = \frac{P_{out}}{V_t}$$

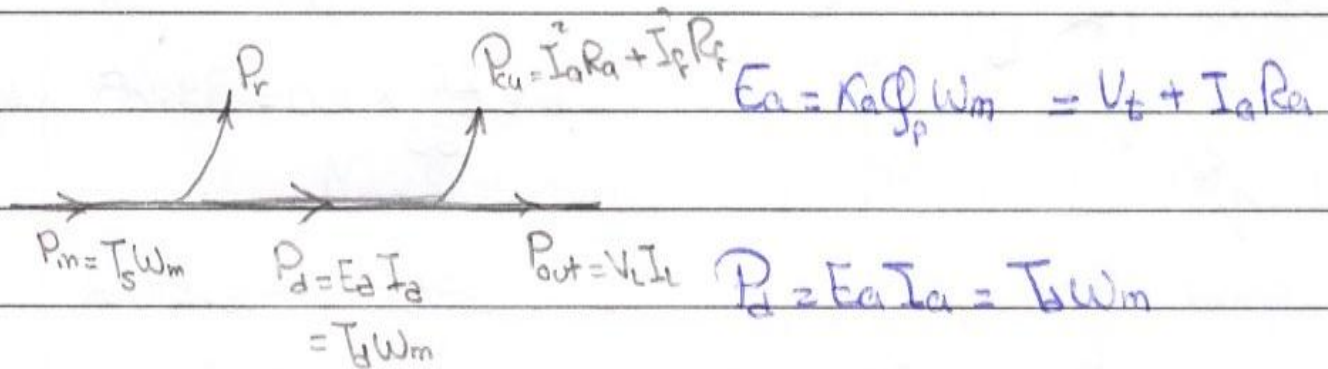

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$


Example 2 (3-11) P. (3-40)

A 50-kW, 120 V shunt generator has $R_a = 0.09 \Omega$

$R_{fw} = 30 \Omega$, $R_{fx} = 15 \Omega$, $N_m = 900 \text{ rpm}$, $P = 5 \text{ kW}$

The generator is delivering the rated load at the rated terminal voltage. Det. a) the generator emf

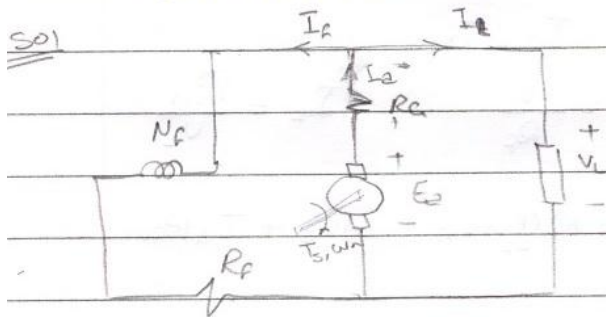T_{sh} b) torque applied c) efficiency. Neglect the armature reaction.



$$R_f = R_{fx} + R_{fw} = 30 + 15 = 45 \Omega$$

$$\omega_m = \frac{2\pi}{60} \times 900 = 94.25 \text{ rad/s}$$

$$I_L = \frac{50 \times 10^3}{120} = 416.67 \text{ A}$$

$$I_f = \frac{V_L}{R_f} = \frac{120}{45} = 2.67 \text{ A}$$

$$\therefore I_a = I_f + I_L = 416.7 + 2.67 = 419.367 \text{ A}$$

$$(a) E_a = V_L + I_a R_a = 120 + (419.367 \times 0.09) = 157.743 \text{ V}$$

$$(b) T_{sh} = \frac{P_m}{\omega_m}$$

$$P_m = P_r + P_a = P_r + E_a I_a = 5 \times 10^3 + (157.743)(419.367) = 71.152 \times 10^3 \text{ watt}$$

$$\therefore T_{sh} = \frac{71.152 \times 10^3}{94.25} = 754.93 \text{ N.m}$$


$$(c) \eta = \frac{P_o}{P_m} \times 100 = \frac{50 \times 10^3}{71.152 \times 10^3} \times 100 = 70.27 \% \sim 70 \%$$

A DC shunt generator driven at speed of 900 rpm. The load draw a current of 200 A for a magnetic flux per pole as 0.1 wb. the machine parameters are armature circuit resistance = 0.1Ω , field circuit resistance = 130Ω , lap connected armature conductor = 300.

draw the generator circuit and its power flow diagram for an eff. of 80%. calculate percentage voltage regulation, field and armature current, rotational and current losses, and the torque applied on the shaft.

Given:- $N_m = 900 \text{ rpm}$ $I_L = 200 \text{ A}$ $\phi_p = 0.1 \text{ wb}$
 $R_a = 0.1 \Omega$ $R_f = 130 \Omega$ Lap connect. $a = p$
 $Z = 300$ conductor

Sol:-

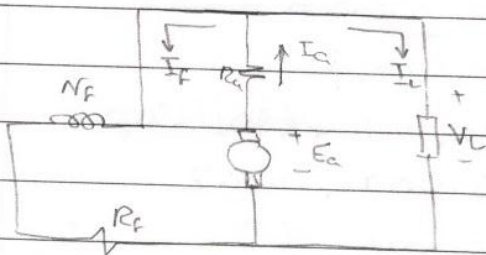


$$\omega_m = \frac{2\pi (900)}{60} = 94.25 \text{ rad/sec}$$

$$E_a = K_a \phi_p \omega_m =$$

$$K_a = \frac{PZ}{2\pi a} = \frac{300}{2\pi} = 47.75$$
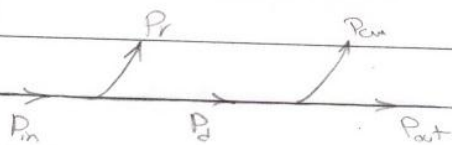
$$\therefore E_a = (47.75)(0.1)(94.25) = 450 \text{ V}$$



$$\begin{aligned} \therefore E_a &= V_L + I_a R_a \\ &= V_L + (I_L + I_f) R_a \\ 450 &= V_L + \left(I_L + \frac{V_L}{R_f}\right) R_a \end{aligned}$$

$$\eta = 80\% = \frac{P_o}{P_{in}} \times 100 =$$

$$\frac{85.93 \times 10^3}{P_{in}} = 0.8$$

$$P_{in} = 107.417 \text{ kW}$$

$$\begin{aligned} 450 &= V_L + (200 \times 0.1) + \left(\frac{0.1}{130}\right) V_L \\ 450 &= V_L + 20 + \left(\frac{0.1}{130}\right) V_L \\ 430 &= 1.000769 V_L \\ V_L &= 429.66 \text{ V} \end{aligned}$$

$$\therefore P_{out} = V_L I_L = 429.66 \times 200 = 85.93 \text{ kW}$$

$$* P_d = E_a I_a = 450 \times (I_f + I_L) = 450 \left(\frac{V_L}{R_f} + 200 \right)$$

$$= 450 \left[\frac{429.99}{130} + 200 \right]$$

$$= 91.488 \text{ kW}$$

$$* \infty P_r = P_{in} - P_d$$

$$= 107.417 - 91.488 = 15.925 \text{ kW}$$

$$* U.R = \frac{E_a - V_t}{V_t} \times 100 = \frac{450 - 429.99}{429.99} \times 100$$

$$= 4.653$$

$$* I_f = V_L / R_f = 429.99 / 130 = 3.3 \text{ A}$$

$$I_a = I_f + I_L = 3.3 + 200 = 203.3 \text{ A}$$

$$* P_{cu} = I_a^2 R_a + I_f^2 R_f = (203.3)^2 (0.1) + (3.3)^2 (130)$$

$$= 4133.089 + 1422.2$$

$$= 5.55 \text{ kW}$$

$$* T_{sh} = \frac{P_{in}}{\omega_m} = \frac{107.417 \times 10^3}{94.25} = 1139.7 \text{ N.m}$$


10/10/2014

• Short Shunt




$$I_g = I_L$$

$$V_c = E_c - I_a R_a - I_c R_c$$

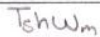


OR "another design"

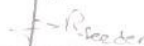

$$I_p R_p$$

or

$$\text{QNO } I_1 = I_3 + I_4$$

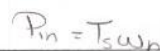

$$= T_{H\omega_m}$$

$$P_o = I_L V_t$$

سازمان چوبی بوقل اندر یک CT-Series ال ۶۰ فی (۱) Seeder

$$\text{ii } E_2 = R_a I_a + R_g I_g + I_L R_{\text{feeder}} + V_t$$

$$P_{cu} = I_a^2 R_{\text{rod}} + I_a^2 R_a + I_f^2 R_f + I_s^2 R_s + I_d^2 R_d$$

Example

A 240V, short-shunt, cumulative compound generator is rated at 100A, the shunt field current is 3A. It has an armature resistance of 50mΩ, a series field resistance of 10mΩ, a field diverter resistance of 40mΩ, and a rotational loss of 2kW, the generator is connected to the load via a feeder R_{fe} of 30mΩ resistance, when the generator is supplying the full load at the rated voltage, determine its efficiency. Draw the power-flow diagram to show the power distribution.



Given $V_L = 240V$ $I_L = 100A$

$I_f = 3A$ $R_a = 50m\Omega$

$R_s = 10m\Omega$ $R_d = 40m\Omega$

$P_r = 2kW$ $R_{fe} = 30m\Omega$

$R_{fe} = 30m\Omega$

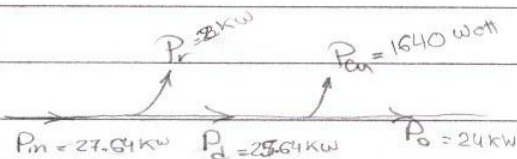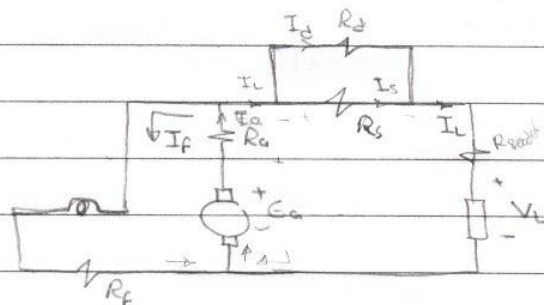

$$P_o = I_L V_L = 240 \times 100 = 24 \text{ kW}$$

$$I_a = I_f + I_L$$

$$I_a = 3 + 100 = 103 \text{ A}$$

Current divider

$$I_s = \frac{R_d}{R_d + R_s} I_L = \frac{0.04}{0.04 + 0.01} \times 100 = 80 \text{ A}$$

$$\therefore I_d = I_L - I_s = 100 - 80 = 20 \text{ A}$$

$$\therefore \eta = \frac{P_o}{P_{in}} \times 100$$

$$= \frac{24 \times 10^3}{27.64 \times 10^3} \times 100 = 93.58\%$$

$$P_{cu} = I_a^2 R_a + I_f^2 R_f + I_s^2 R_s + I_d^2 R_d +$$

$$I_{fe}^2 R_{fe}$$

watt

$$E_a = I_a R_a + I_s R_s + V_L + R_{fe} I_L = (103)(0.05) + (80)(0.01) + 240 + (0.03)(100) = 248.95 \text{ V}$$


if given N

$$\therefore T_g = \frac{P_{in}}{\omega_n}$$

$$P_d = E_a I_a = 248.95 \times 103 = 25.64 \text{ kW}$$

$$\therefore P_{in} = P_d + P_r = 25.64 \times 10^3 + 2 \times 10^3 = 27.64 \times 10^3 \text{ watt}$$

Direct current Motor.

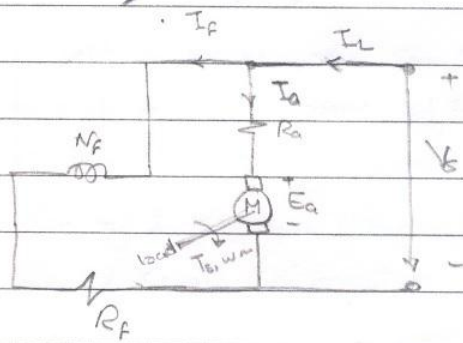

Es back emf

$$I_L = I_f + I_a$$

$$P_{in} = V_s I_L$$


$$P_{out} = T_s \omega_m$$

$$V_s = I_f R_f$$

$$E_a = V_s - I_a R_a$$

$$E_a = K_a \Phi_p \omega_m$$

"eqn. of shunt motor"

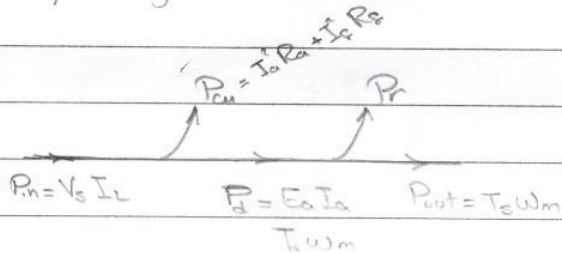


$$\omega_m = \frac{V_s - R_a I_a}{K_a \Phi_p}$$

$$V_R = \frac{V_{mload} - V_{f.L} \times 100}{V_{f.L}}$$

speed regulation
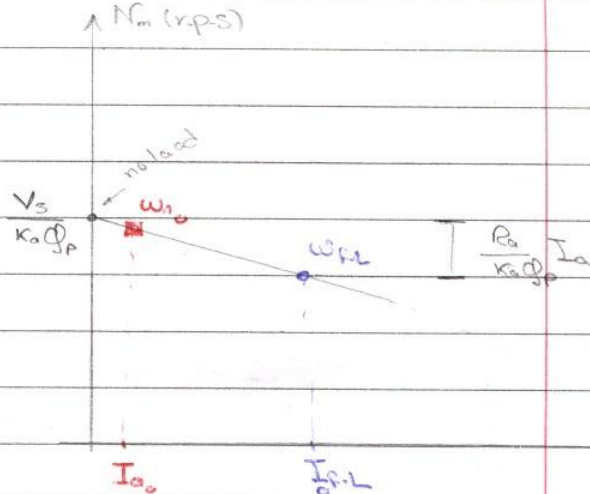
$$= \frac{N_{m.L} - N_{f.L} \times 100}{N_{f.L}}$$



Power Flow diag. 1- at no load $\Rightarrow P_{out} = 0$

2- at full load \Rightarrow

Power flow diagram

speed current char's

Sketch speed current char's.

No-load speed

$$\omega_{m.L} = \frac{V_s}{K_a \Phi_p}$$

Speed drop

$$\Delta \omega = \frac{R_a}{K_a \Phi_p} I_a$$

$$I_{st} = \frac{V_s}{R_a} \text{ "starting current"}$$

step

$$\frac{E_{a.L}}{E_{a.f.L}} = \frac{N_{m.L}}{N_{m.f.L}} \text{ (constant } K_a \Phi_p)$$

Example (4.2) A 240 V shunt motor takes a current of 3.5 A on no load. the armature ct. resistance is 0.5Ω and the shunt-field-winding resistance is 160Ω . When the motor operates at full load at 2400 rpm, it takes 24 A. Determine (a) I_{FL} (b) torque developed and useful torque (T_d & T) (c) no-load speed (d) percent speed regulation. sketch power-flow diagram for each operating condition.

Given:- $V_s = 240 \text{ V}$ $I_L = 3.5 \text{ A}$ $R_a = 0.5 \Omega$
 $R_f = 160 \Omega$ $N_{FL} = 2400 \text{ rpm}$ $I_{LFL} = 24 \text{ A}$

Sols:-

At No-load

$$\therefore I_{f_{n.L}} = V_s / R_f = 240 / 160 = 1.5 \text{ A}$$



$$\therefore I_a = I_L - I_f = 3.5 - 1.5 = 2 \text{ A}$$

$$E_a = V_T - I_a R_a$$

$$= 240 - (2)(0.5) = 239 \text{ V}$$

$$\therefore P_d = E_a I_a = (239)(2) = 478 \text{ watt}$$
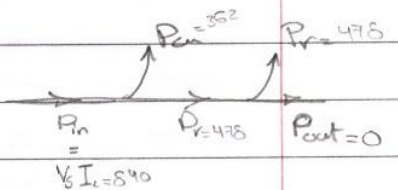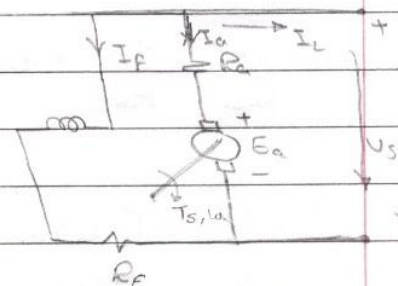
$$\therefore P_r = P_d = 478 \text{ watt} \quad \#$$



$$P_{cu} = I_a^2 R_a + I_f^2 R_f = (2)^2(0.5) + (1.5)^2(160)$$

$$= 2 + 360 = 362 \text{ watt}$$

$$\therefore P_{in} = P_{cu} + P_d = 362 + 478 = 840 \text{ watt}$$

$$P_d = T_d \omega_m$$

at Full load

$$I_f = 240 / 160 = 1.5$$


$$I_{a_{FL}} = I_{L_{FL}} - I_f = 24 - 1.5 = 22.5 \text{ A}$$

$$E_a = V_T - R_a I_a = 240 - (0.5)(22.5) = 228.75 \text{ V}$$

$$P_d = E_a I_a = (228.75)(22.5) = 5.147 \text{ kW}$$

$$\therefore P_{out} = P_d + P_r = 5.147 \times 10^3 + 478 = 4.669 \text{ kW}$$
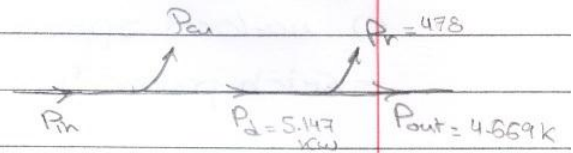
$$\begin{aligned} P_{cu} &= I_a^2 R_a + I_f^2 R_f \\ &= (22.5)^2 (0.5) + (1.5)^2 (160) \\ &= 613.125 \text{ watt} \\ &= P_{in} - P_d \end{aligned}$$



$$P_{in} = V_s I_L = (240)(24) = 5.76 \text{ kW}$$

$$(a) \times \therefore \eta_{cl} = \frac{P_{out}}{P_{in}} \times 100 = \frac{4.669}{5.76} \times 100 = 81.06\%$$

$$(b) \times \quad \begin{aligned} P_d &= T_d \omega_m \\ T_d &= \frac{5.147 \times 10^3}{\frac{2\pi}{60} (2400)} = 20.48 \text{ N.m} \end{aligned}$$

$$T_{sh} = \frac{P_{out}}{\omega_m} = \frac{4.669 \times 10^3}{\frac{2\pi}{60} (2400)} = 18.57 \text{ N.m}$$

$$\begin{aligned} (c) \quad N_{aL} &= 2400 \times \frac{E_{a nL}}{E_{a fL}} = 2400 \times \frac{239}{228.75} \\ &= 2507.54 \text{ (rpm)} \end{aligned}$$

$$\begin{aligned} (d) \quad \text{speed regulation} &= \frac{N_{aL} - N_{sL}}{N_{sL}} \times 100 = \frac{2507 - 2400}{2400} \times 100 \\ &= 4.48\% \end{aligned}$$

2018/5/4
Wazir

Exercise:

(4-5) A 120 V shunt motor takes 4 A when it operates at ~~operates~~ its no-load speed of 1200 rpm. Its armature winding resistance is 0.8Ω and the shunt field resistance is 60Ω . Determine the efficiency and the speed of the motor when it delivers its rated load of 2.4 kW.

Given:-

$$V_s = 120 \text{ V}$$

$$I_L = 4 \text{ A}$$

$$N_{n.L} = 1200 \text{ rpm}$$

$$R_a = 0.8 \Omega$$

$$R_s = 60 \Omega$$

→ at no. load



$$P_{out} = 0$$

$$\therefore P_d = P_r$$

$$P_d = E_a n_L \times I_a n_L$$

$$E_a = V_s - I_a R_a$$

$$I_a = I_L - I_f$$

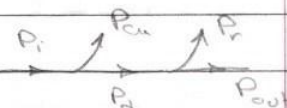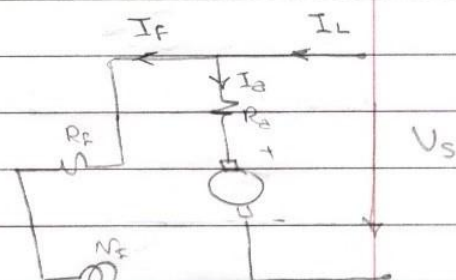

$$\therefore E_a = V_s - \left[I_L - \frac{120}{60} \right] 0.8$$

$$= 120 - (4 - 2) \times 0.8 = 118.4 \text{ V}$$

$$\therefore P_d = P_r = 118.4 \times 2 = 236.8 \text{ W}$$

→ At full load

$$E_{a.FL} = V_s - I_{a.FL} R_a$$

$I_{a.FL}$ is unknown

$$P_d = I_a E_a = I_a V_s - I_a^2 R_a$$

$$P_{d.FL} = 120 I_{a.FL} - 0.8 I_{a.FL}^2$$

$$P_{d.FL} = P_r + P_{out} = 236.8 + 2.4 \times 10^3 = 2636.8$$

$$\therefore 2636.8 = 120 I_{a.FL} + 0.8 I_{a.FL}^2 = 0$$

$$I_a = 123.25$$

$$I_a = 26.7$$

rejected

$$\therefore E_a = \frac{P_{d.FL}}{I_{a.FL}} = 98.7 \approx 99 \text{ V}$$

$$\therefore I_L = I_a + I_f = 26.7 + 2 = 28.75 \text{ A}$$

$$P_{in} = V_s I_L = (120)(28.75) = 3450 \text{ watt}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100 = 69.56 \%$$

$$E_{a.n.L} = \frac{N_m n.L}{N_m f.L}$$

$$E_{a.f.L} = \frac{N_m f.L}{N_m n.L}$$

$$N_{m.f.L} = \frac{99 \times 1200}{118.4}$$

$$= 1003.37$$

Exercise (4.6)

A 220V shunt motor draws 10A at 1800 rpm. The armature-circuit resistance is 0.2Ω , and the field-winding resistance is 440Ω . The rotational loss is 180W. Determine

- (a) back emf (b) driving torque (c) shaft torque
(d) efficiency of the motor.


Sol:-

Given:-


$$V_s = 220\text{ V} \quad I_L = 10\text{ A} \quad N = 1800$$

$$R_a = 0.2\Omega \quad R_f = 440\Omega$$

$$P_r = 180$$

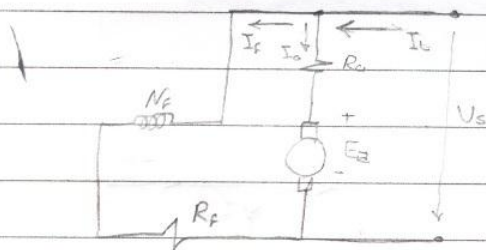
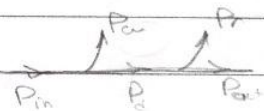
$$\therefore I_f = V_s / R_f = \frac{220}{440} = 0.5\text{ A}$$



$$I_a = I_L - I_f = 10 - 0.5 = 9.5\text{ A}$$

$$(a) \quad E_b = V_s - I_a R_a = 220 - (9.5)(0.2) = 218.1\text{ V}$$

$$(b) \quad P_a = E_b I_a = (218.1)(9.5) = 2.07195\text{ kW}$$

$$T_a = \frac{P_a}{\omega} = \frac{2.07195 \times 10^3}{\frac{2\pi(1800)}{60}} = 10.942\text{ N.m}$$

$$P_{in} = V_s I_L = (220)(10) = 2200\text{ watt}$$

$$P_{out} = P_a - P_r = 2.07195 \times 10^3 - 180 = 1.89195\text{ kW}$$

$$(c) \quad \therefore T_{sh} = \frac{P_{out}}{\omega} = \frac{1.89195 \times 10^3}{\frac{2\pi(1800)}{60}} = 10.037\text{ N.m}$$

$$(d) \quad \eta = \frac{P_o}{P_{in}} \times 100 = \frac{1.89195\text{ kW}}{2200} = 85.99\%$$

A dc shunt motor drive a load for a supply voltage of 240 V. the armature current is measured as 25 A. and the rated speed is accounted to be 2200 rpm. The machine resistances are 0.8 ohm for the armature and 120 ohm for the field winding

- draw the motor circuit and its power flow diagram

- calculate the machine const. $k_a \phi_f$, the no load speed N_{nl}

- the torque on the shaft for a rotational losses of 100W

- and motor efficiency.

- sketch without any scale the speed current characteristics showing the rated and no load value.

P.L. \Rightarrow I_a کی طرف سے


Given:- $V_s = 240V$

$I_a = 25A$

$N = 2200 \text{ rpm}$

$R_a = 0.8 \Omega$

$R_f = 120 \Omega$

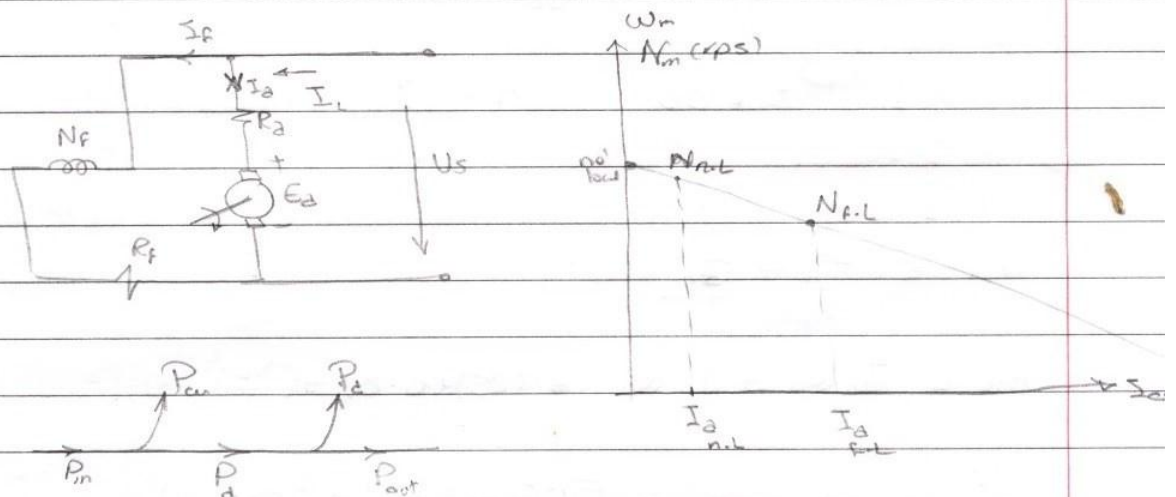

$$E_a = k_a \phi_f \omega_m = V_t - I_a R_a$$

$$k_a \phi_f = \frac{240 - (25)(0.8)}{\frac{2\pi}{60} \times 2200} = 0.955 \text{ (V/rad/sec)}$$

$$k_a \phi_f = 0.955 \text{ (V/rad/sec)}$$

$$\omega_m = \frac{V_s}{k_a \phi_f} - \frac{R_a}{k_a \phi_f} I_a$$

$$\text{at no load } \omega_m = \frac{V_s}{k_a \phi_f} = \frac{240}{0.955} = 251.327 \text{ rad/sec}$$

P.2 السرعة rated speed $N_{f.L} \leftarrow$ rated speed

$$N_{m_{nl}} = 60 \times 251.3 / 2\pi = 2400 \text{ rpm}$$

At full load

$$P_d = E_a I_a = 240 \times 25 = 6000 \text{ W}$$

$$\therefore E_a = V_t - I_a R_a = 240 - (25)(0.8) = 220 \text{ V}$$

$$P_d = 220 \times 25 = 5.5 \text{ kW}$$

$$P_{out} = P_d - P_r = 5.5 \text{ kW} - 100 \text{ W} = 5.4 \text{ kW}$$

$$T_{sh} = \frac{P_{out}}{\omega} = \frac{5.4 \times 10^3}{\frac{2\pi}{60} (2200)} = 23.439 \text{ N.m}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100$$

$$P_{in} = P_{cu} + P_d$$

$$P_{cu} = I_a^2 R_a + I_f^2 R_f = (25)^2 (0.8) + \left(\frac{V_L}{R_L}\right)^2 120$$

$$= 500 + 480 = 980 \text{ W}$$

$$\therefore P_{in} = P_d + P_{cu} = 5.5 \times 10^3 + 980 = 6.48 \text{ kW}$$

$$\eta = \frac{5.4}{6.48} \times 100 = 84.87 \%$$

Exercise (4-7)

A 220V shunt motor draws 10A at 1800 rpm. The armature circuit resistance is 0.2Ω and the field winding resistance is 440Ω . The rotational loss is 180W.

If the torque developed by the motor is 20 N.m.

Determines: a) speed (N) b) line current (I_L)



c) efficiency.

Given: $V_t = 220V$, $I_L = 10A$

$N = 1800 \text{ rpm}$ $R_a = 0.2\Omega$

$R_f = 440\Omega$ $P_r = 180W$

$P_d = 20 \text{ N.m}$

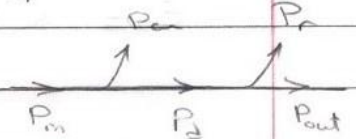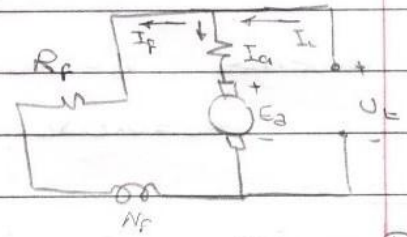

Soln

جيبى ان T_s فى حالة الـ full load
and Power

و جيبى الـ speed
at no-load.

Examples:-

DC-shunt motor drive a load for supply voltage 240V. The armature current = 25A The rated speed = 2200 rpm $R_a = 0.8 \Omega$ $R_f = 120 \Omega$ calculates:-

1- Machine const. ($K_a \phi_p$)

2- N_m Int

3- $T_s \rightarrow P_r = 100W$.

Given:- $V_t = 240V$

$I_a = 25A$


$N = 2200 \text{ rpm}$
F.L

$R_a = 0.8 \Omega$

$R_f = 120 \Omega$

sols:-

$$E_a = K_a \phi_p \omega_m$$

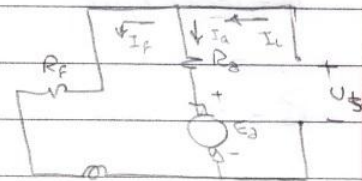

$$E_a = V_t - I_a R_a = 240 - (25 \times 0.8) = 220V$$

$$\therefore K_a \phi_p = \frac{E_a}{\omega_m} = \frac{220}{\frac{2\pi}{60} (2200)} = 0.9549 \text{ V(rad/sec)}$$

→ At No-load.

$$P_o = 0$$

$$\therefore P_r = P_d = E_a I_{a,n.l.}$$

$$E_{a,n.l.} = V_t - I_{a,n.l.} R_a$$

$$P_{d,n.l.} = I_{a,n.l.} (240) - I_{a,n.l.}^2 (0.8)$$

$$100 - 240 I_{a,n.l.} + 0.8 I_{a,n.l.}^2$$

$$I_a = 299.58$$


$$I_{n.l.} = 0.417$$

rejected

$$\therefore E_{a,n.l.} = 240 - (0.417)(0.8) = 239.66V$$

$$\therefore \frac{E_{a,n.l.}}{E_{a,n.l.}} = \frac{N_{n.l.}}{N_{n.l.}}$$
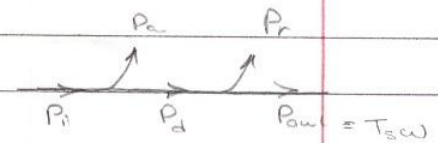
$$\therefore N_{n.l.} = \frac{(239.66)(2200)}{220} = 2396.66$$



$$\therefore P_{act} = P_d - P_f$$

$$= (220)(25) - 100$$

$$= 400 \text{ watt}$$


$$\therefore T_s = \frac{P_{act}}{\omega_{f.l.}}$$

$$= \frac{400}{\frac{2\pi}{60} (2200)}$$

$$= 1.736 \text{ Nm}$$

سynchronous generator

Synchronous Generator.

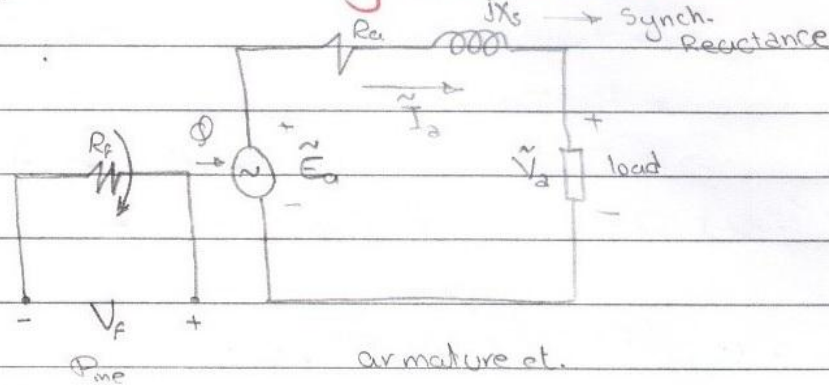

jX_s : Synchronous reactance

R_a : Synchronous resistance

$$\tilde{E}_a = \tilde{V}_a + \tilde{I}_a(R_a + jX_s)$$

$$\omega_s = \frac{2\pi}{60} N_s$$

$$N_s = \frac{120f}{P}$$

$$P_m = \omega_s T_{sh} + I_f R_f$$

$$P_d = \frac{3V_a E_a \sin \delta}{X_s}$$


$$V_a R\% = \frac{E_a - V_a}{V_a} \times 100$$

$$\eta = \frac{3V_a I_a \cos \theta}{3V_a I_a \cos \theta + P_o + 3I_o^2 R_a}$$

$$\begin{aligned} P_m &= T_{sh} \omega_s + I_f^2 R_f \\ &\text{or } T_{sh} \omega_s + V_f I_f \\ P_r &= I_f^2 R_f \\ P_{cu} &= 3I_a^2 R_a \\ P_d &= \frac{3E_a V_a}{X_s} \sin \delta \\ P_o &= 3V_a I_a \cos \theta \end{aligned}$$

$$\begin{aligned} P_m &= V_f I_f \\ P_m &= T_{sh} \omega_m \\ P_d &= 3I_o E_a \cos \theta \\ P_r + P_{st} &= P_o \\ P_{cu} &= 3I_o^2 R_a \\ P_o &= 3V_a I_a \cos \theta \end{aligned}$$

$$V_{ph} = \frac{V_{line}}{\sqrt{3}}$$

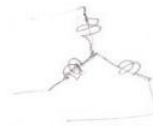


V.V.I Example (2.6) :-

A 9-KVA, 208-V, three phase, Y-Connected, Synchronous generator has a winding resistance of 0.1Ω /phase and a Synchronous reactance of 5.6Ω /phase. Determine its voltage regulation when the power factor of the load is (a) 80% lagging (b) unity (c) 80% leading.

Given:- $S = P = 9 \text{ K}$ $V_a = 208 \text{ V}$ Y connection
 $R_a = 0.1 \Omega$ /phase $X_s = 5.6 \Omega$ /phase

Sols:-
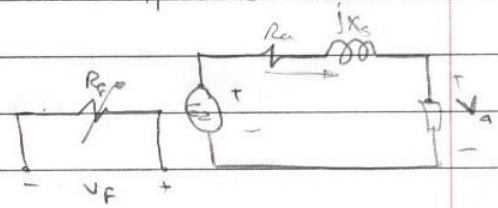
$$\therefore V_{phase} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$



$$V.R = \frac{E_a - V_t}{V_t}$$

$$E_a = V_t + I_a(R_a + jX_s) \\ = 120 + I_a(0.1 + j5.6)$$

مع تغير P.F. الـ V_t ثابت
 الـ E_a يتغير هو الـ E_a

$$\rightarrow I_a = \frac{S}{3V_a} = \frac{9 \times 10^3}{3 \times 120} = 25 \text{ A}$$

بعض الـ E_a يتغير الـ P.F. حسب
 الـ E_a عند كل حالة.

$$\therefore E_a = 120 + 25(0.1 + j5.6) \\ = 122.5 + j140 \text{ V}$$


بسط الزاوية مع الـ E_a
 في حساب E_a

(a) at 80% lagging

$$\therefore \text{P.F.} = 0.8 \rightarrow \theta = -36.86^\circ \quad \cos^{-1} 0.8 = 36.86^\circ$$

$$\therefore E_a = 120 + 25 \angle -36.86^\circ (0.1 + j5.6) \\ = 120 + (25 \angle -36.86^\circ)(5.6 \angle 88.97^\circ) \\ = 120 + 140 \angle 52.106^\circ = 205.988 + j110.48 \\ = 233.74 \angle 28.206^\circ \text{ V}$$

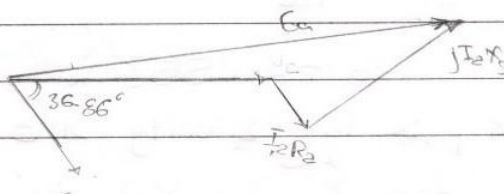
$$\therefore V.R = \frac{E_a - V_t}{V_t} = \frac{233.74 - 120}{120} \times 100 \\ = 94.8\%$$



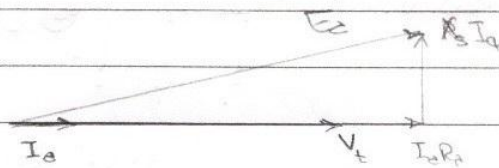(b) unity power factor $\theta = 0^\circ$


$$\begin{aligned}\tilde{E}_a &= 120 + (0.1 + j5.6) 25 \angle 0^\circ \\ &= 122.5 + j140 = 186 \angle 48.8^\circ\end{aligned}$$

$$\therefore V.R = \frac{E_a - V_t}{V_t} \times 100 = \frac{186 - 120}{120} \times 100 = 55\%$$



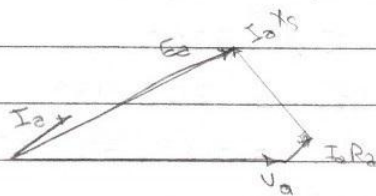
(c) 80% leading - 0.8 $\theta = +36.86^\circ$

$$\begin{aligned}\therefore E_a &= V_t + 25 \angle 36.86^\circ (0.1 + j5.6) \\ &= 120 + 25 \angle 36.86^\circ (0.1 + j5.6) \\ &= 120 + (25 \angle 36.86^\circ)(5.6 \angle 88.975^\circ) \\ &= 120 + 140 \angle 125.835^\circ \\ &= 38.034 + j113.44 = 119.693 \angle 71.47^\circ \text{ V}\end{aligned}$$



$$\begin{aligned}V.R &= \frac{E_a - V_t}{V_t} \times 100 = \frac{119.693 - 120}{120} \times 100 \\ &= -0.2553\%\end{aligned}$$

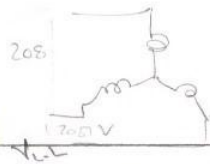في ال lead ال (c) +ve ال V.R لم lag & unity ال
Z_s ال V.D ال



E_a is induced emf or exciting voltage.

Given power Example (2-7)

for 3ph A 9-kVA, 208V, 1200 rpm, three phase, 60 Hz, Y connected Synchronous generator has a field winding resistance of 4.5Ω . the armature-winding impedance is $0.3 + j5 \Omega$ /phase when the generator operates at its full load and 0.8 pf. lagging the field winding current is 5A. the rotational loss is 500w Determine (a) the voltage regulation.

(b) efficiency of the generator

(c) the torque applied by the prime mover.

Given $S = 9 \times 10^3 = 3 V_a I_a$

$$V_a = \frac{208}{\sqrt{3}} = 120 \text{ V}$$

$$R_a = 0.3 \Omega \quad X_s = 5 \Omega$$


$$R_f = 4.5 \Omega$$

$$\text{PF} = 0.8 \text{ lag}$$

$$I_f = 5 \text{ A}$$

$$\theta = -36.86^\circ$$

$$P_r = 500 \text{ W}$$

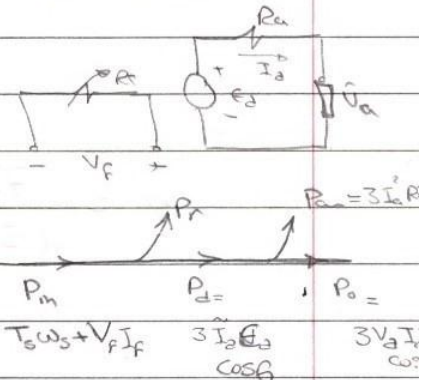

Sol:-

$$V_a = 120 \text{ V}$$

$$S = 3 V_a I_a$$

$$I_a = \frac{9 \times 10^3}{3 \times 120} = 25 \text{ A}$$

$$I_a = 25 \angle -36.86^\circ \text{ A}$$

$$E_a = V_t + I_a (R_a + jX_s)$$

$$= 120 + 25 \angle -36.86^\circ (0.3 + j5)$$

$$= 120 + (25 \angle -36.86^\circ) (5.186.566)$$

$$E_a = 120 + 125 \angle 49.706^\circ = 200.839 \angle 95.34^\circ$$

$$\% \text{ U.R.} = \frac{E_a - V_t}{V_t} = \frac{200.839 - 120}{120} = 67.35\%$$

$$P_o = 3 V_a I_a \cos \theta = 3 \times 120 \times 25 \times 0.8 = 7200 \text{ W}$$

$$= S \times 0.8 = 7200 \text{ W} = 7.2 \text{ kW}$$

$$\eta = \frac{P_o}{P_m} \times 100$$

$$P_m = T_d \omega_s + V_f I_f$$

$$V_f I_f = 5 (5 \times 4.5) = 112.5 \text{ W}$$

$$P_d = 3 E_a I_a \cos \delta = 3(200.893)(25)(0.8) \\ = 7762.4 \text{ W}$$

$$\therefore P_{in} = P_r + P_d$$

$$T_s \omega_s = 500 + 7762.4 - 112.5 \\ = 8149.9$$

$$\therefore T_s = \frac{8149.9}{\frac{2\pi}{60} \times 1200} = 64.85 \text{ N.m}$$

$$\eta = \frac{7.2 \text{ K} \times 100}{(500 + 7762.4)} = 87 \%$$

<http://www.com-dep.tk/>